

Worksheet 5
Boolean Logic

Draw a circuit representing a Boolean expression $(y' \wedge z') \vee [(w \wedge x') \wedge y']'$.