

Worksheet 5

Boolean Logic

Draw a circuit representing a Boolean expression

$$(y' \wedge z') \vee [(w \wedge x') \wedge y']'$$

